

Experiment - 4

Current Source, Current Mirror, and Differential Pair

Report by Prasann Viswanathan - 190070047

1. BJT Current Source

a. ngspice code:

```
Prasann Viswanathan 190070047 BJT Current Source Analysis



.include zener_B.txt
.model bc557a PNP IS=10f BF=100 ISE=10.3f IKF=50m NE=1.3
+ BR=9.5 VAF=80 IKR=12m ISC=47p NC=2 VAR=10 RB=280 RE=1 RC=40
+ tr=0.3u tf=0.5n cje=12p vje=0.48 mje=0.5 cjc=6p vjc=0.7 mjc=0.33 kf=2f

q1 4 3 2 bc557a
vcc 1 0 12
v1 5 0 0
xz 3 1 DI_1N4734A
re 1 2 4.7k
rb 3 0 2.2k
rl 4 5

*analysis commands
.dc rl 1k 10k 1k
.control
run

*display commands
plot i(v1)
plot v(2) v(3) v(4)
.endc
.end
```

b. Results

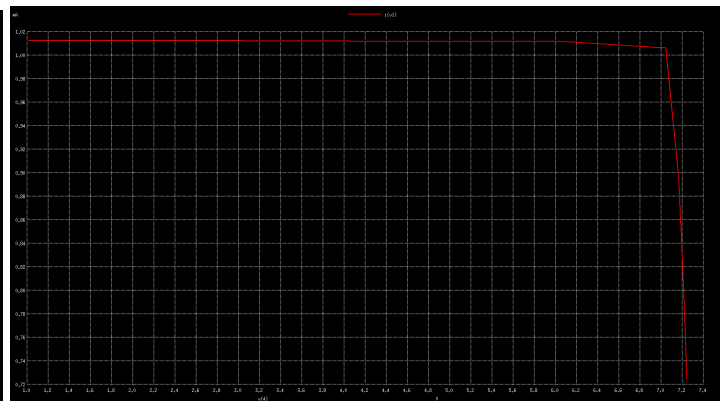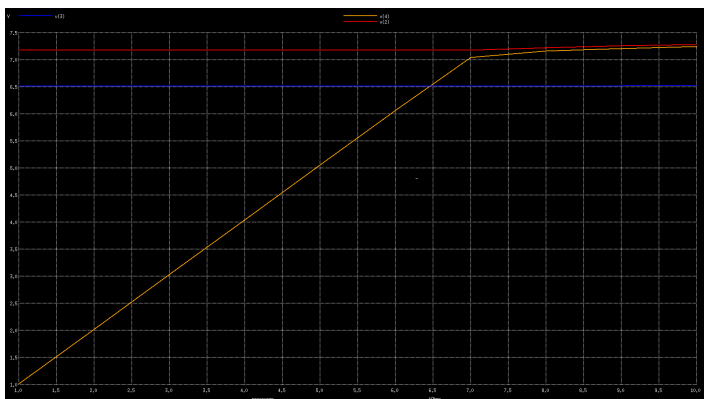

c. Learning Outcomes

I learnt how to do the DC analysis of a current source circuit (something which was new for us). I also saw that the values matched sufficiently with NGSPICE simulations as well. Finally I learnt that a practical current sources' current value decreases with increasing output voltage. (DC analysis below)

$i(v1) = 1.012823e-03$

$v(2) = 7.176963e+00$

$v(3) = 6.516322e+00$

$v(4) = 1.012823e+00$

2. BJT Current Mirror based Current Source

a. ngspice code:

```
Prasann Viswanathan 190070047 BJT Current Mirror


.model bc547a NPN IS=10f BF=200 ISE=10.3f IKF=50m NE=1.3
+ BR=9.5 VAF=80 IKR=12m ISC=47p NC=2 VAR=10 RB=280 RE=1 RC=40
+ tr=0.3u tf=0.5n cje=12p vje=0.48 mje=0.5 cjc=6p vjc=0.7 mjc=0.33 kf=2f

q1 2 2 0 bc547a
q2 3 2 0 bc547a
vcc 1 0 12
vo 3 0
r 1 2 10k

*analysis commands
.dc vo 1 5 0.5
.control
run

*display commands
plot i(vo) i(vcc)
.endc
.end
```

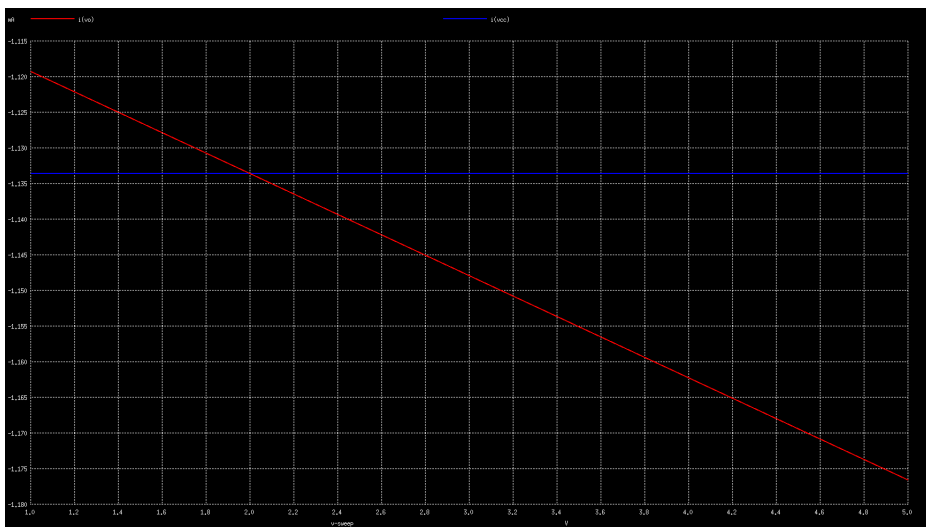b. Results (plot is for $V_a = 80V$ case)



```
i(vcc) = -1.13359e-03
i(vo) = -1.11923e-03
v(2) = 6.641060e-01
```

c. Learning outcomes

For Q1, $V_{CE} = V_{BE} = 0.7V$. For $V_o = 1V$, $\beta = 100$, and $V_A = 80V$: $I_{ref} = (V_{CC} - V_{BE})/R = 1.13m A$

$I_o = I_{ref}/(1+2/\beta) \cdot (1+ V_o - V_{BE}/V_A) = 1.167m A$

For the values $V_o = 1V$, $\beta = 100$, and $V_A = 80V$, the value of I_o obtained is $1.119mA$ which is reasonably close to the value of $I_o = 1.167m A$ calculated using analysis.

(Note that the currents in my analysis are negative as NGSPICE convention is to give negative sign to currents emanating from an Anode. Adding a dummy voltage source would lead to lengthy code)

I learnt that the formulae is a very good approximation for actual simulated results and the effect of early voltage of the transistors is clearly seen in our plot as the magnitude rises when V_o is increased.

3. Differential Pair (Small Signal Analysis)

a. ngspice code:

```
Prasann Viswanathan 190070047 BJT Differential Amplifier


.model bc547a NPN IS=10f BF=200 ISE=10.3f IKF=50m NE=1.3
+ BR=9.5 VAF=80 IKR=12m ISC=47p NC=2 VAR=10 RB=280 RE=1 RC=40
+ tr=0.3u tf=0.5n cje=12p vje=0.48 mje=0.5 cjc=6p vjc=0.7 mjc=0.33 kf=2f

q1 4 6 8 bc547a
q2 5 7 8 bc547a
vcc 1 0 12
vin1 10 0 dc sin(0 10m 1k 0 0 0)
vin2 11 0 0
ve 9 0 -12
rc1 1 2 6.8k
rc2 1 3 6.8k
rb1 10 6 1k
rb2 11 7 1k
re 9 8 10k
vo1 2 4 0
vo2 3 5 0

*analysis commands
.tran 10u 10m
.control
run

*display commands
plot v(4) v(5)
.endc
.end
```

b. Results (Vo1 and Vo2 vs time)

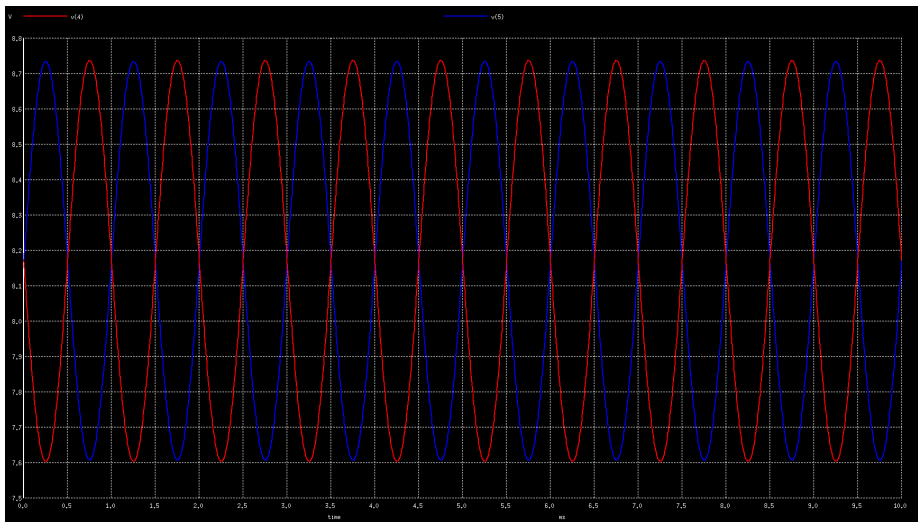

```
i(vo1) = 5.630784e-04
i(vo2) = 5.630784e-04
i(ve) = 1.135396e-03
v(4) = 8.171067e+00
v(5) = 8.171067e+00
v(8) = -6.46041e-01
```

c. Learning outcomes

I learnt the gain expression for a single side is $-gmRc/2$ and this matches reasonably well with the experimental results as well. There is a phase shift of exactly π between the two V_{out} s, as explained in the lab lecture.

d. Doubts/Clarifications

On doing small signal analysis, we get the gain expression (ignoring R_b) to be $-gmRc/(1+2gmR_e)$. Why?

4. Differential Pair (Large Signal Characteristics)

a. ngspice code:

```
Prasann Viswanathan 190070047 BJT Differential Amplifier


.model bc547a NPN IS=10f BF=200 ISE=10.3f IKF=50m NE=1.3
+ BR=9.5 VAF=80 IKR=12m ISC=47p NC=2 VAR=10 RB=280 RE=1 RC=40
+ tr=0.3u tf=0.5n cje=12p vje=0.48 mje=0.5 cjc=6p vjc=0.7 mjc=0.33 kf=2f

q1 4 6 8 bc547a
q2 5 7 8 bc547a
vcc 1 0 12
vin1 10 0 0
vin2 11 0 0
ve 9 0 -12
rc1 1 2 6.8k
rc2 1 3 6.8k
rb1 10 6 1k
rb2 11 7 1k
re 9 8 10k
vo1 2 4 0
vo2 3 5 0

*analysis commands
.dc vin1 -1 1 0.01
.control
run

*display commands
plot v(4) v(5)
.endc
.end
```

b. Results

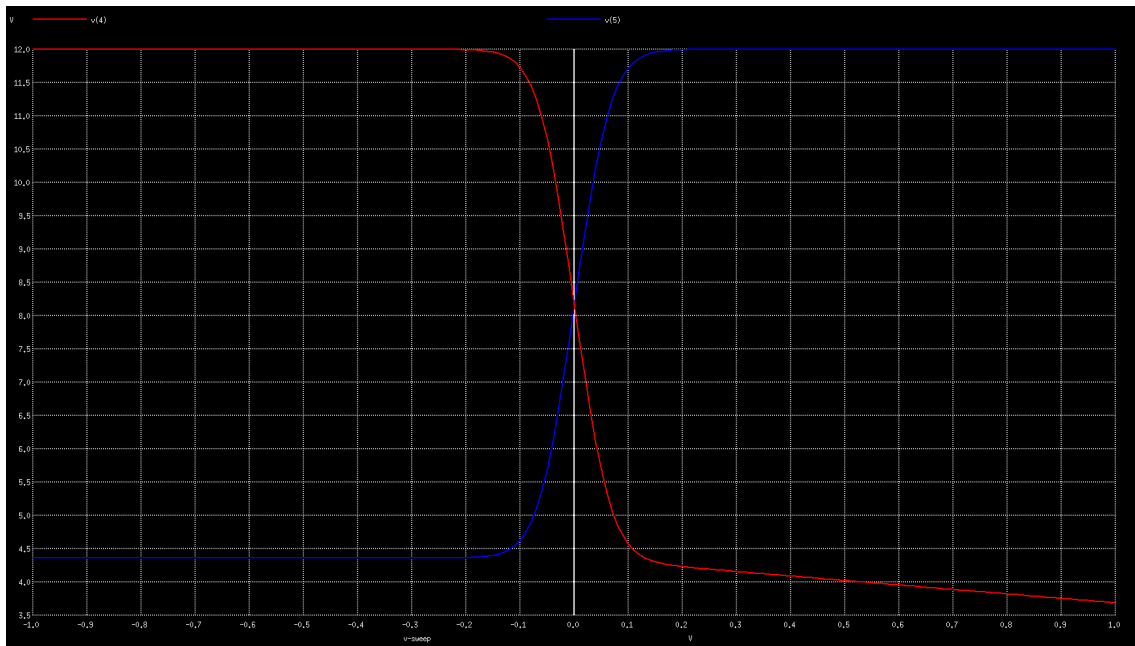

c. Learning outcomes

When the value of V_{in} goes beyond the rough range (-0.1 to 0.1) then beyond that range, the values of V_{o1} and V_{o2} (V_{c1} and V_{c2}) remain saturated. Also, there is asymmetry between values of V_{c1} and V_{c2} for $V_{in} > 0.1$, shown by the negative slope in the red graph.