

# Experiment - 1


## Familiarization with NGSPICE Circuit Simulator and Lab Equipment

---

Report by Prasann Viswanathan - 190070047

### 1. RC Integrator

a. Circuit Diagram:

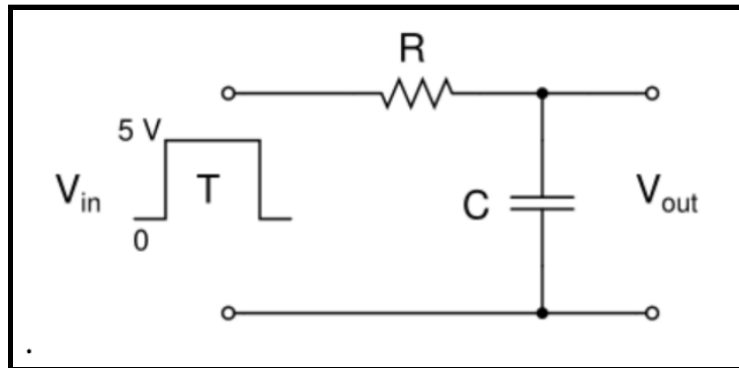

b. ngspice code:

```
Prasann Viswanathan 190070047 RC Integrator
```



```
r1 1 2 10k
c1 2 0 0.1u
*v_in 1 0 pulse(0 5 0.1u 0 0 10m 20m)
v_in 1 0 pulse(0 5 0.1u 0 0 1m 2m)
```

```
*analysis command
*.tran 10u 40m
.tran 10u 10m
.control
run
```

```
*display commands
plot v(2) v(1)
.endc
.end
```

---


c. Results:

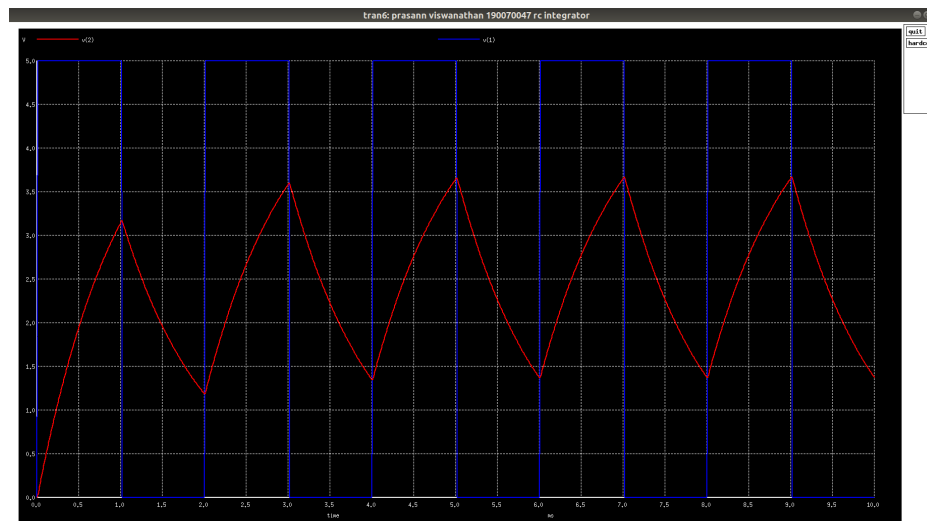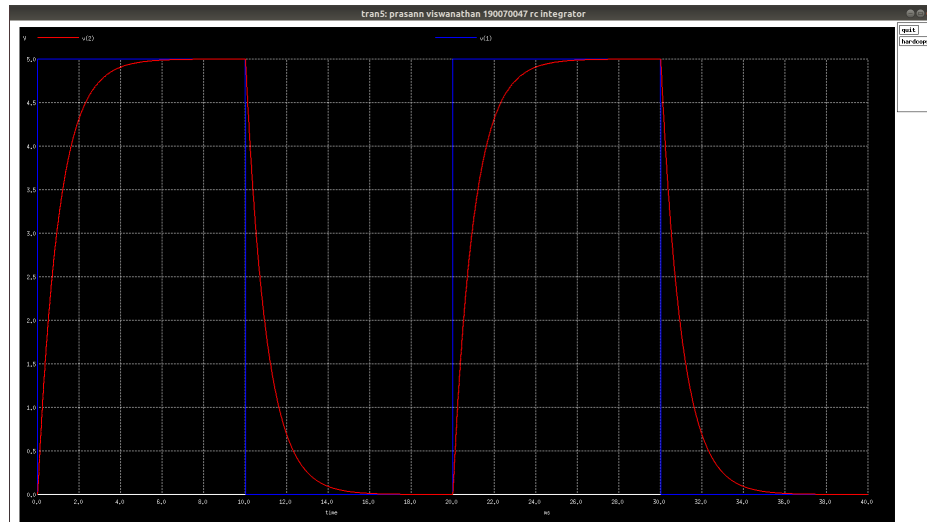

---

## 2. RC Differentiator

a. Circuit Diagram:

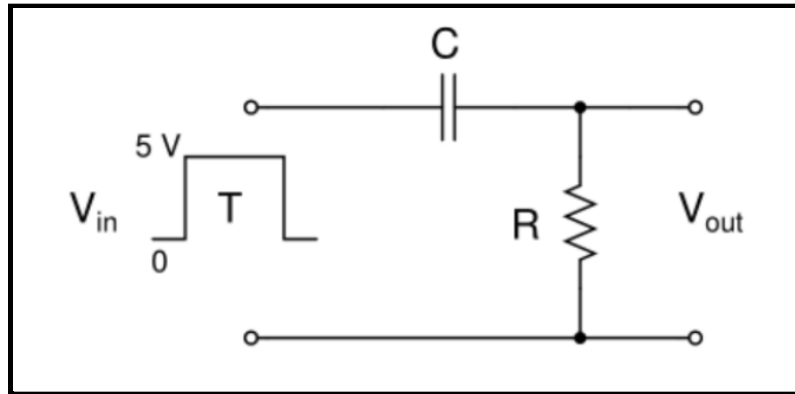

b. ngspice code:

```
Prasann Viswanathan 190070047 RC Differentiator
```

```
r1 2 0 1k
c1 1 2 0.1u
*v_in 1 0 pulse(0 5 1u 0 0 10m 20m)
v_in 1 0 pulse(0 5 1u 0 0 1m 2m)
```

```
*analysis commands
```

```
*.tran 0.1u 40m
```

```
.tran 0.1u 10m
```

```
.control
```

```
run
```



```
*display commands
```

```
plot v(2) v(1)
```

```
.endc
```

```
.end
```


c. Results:

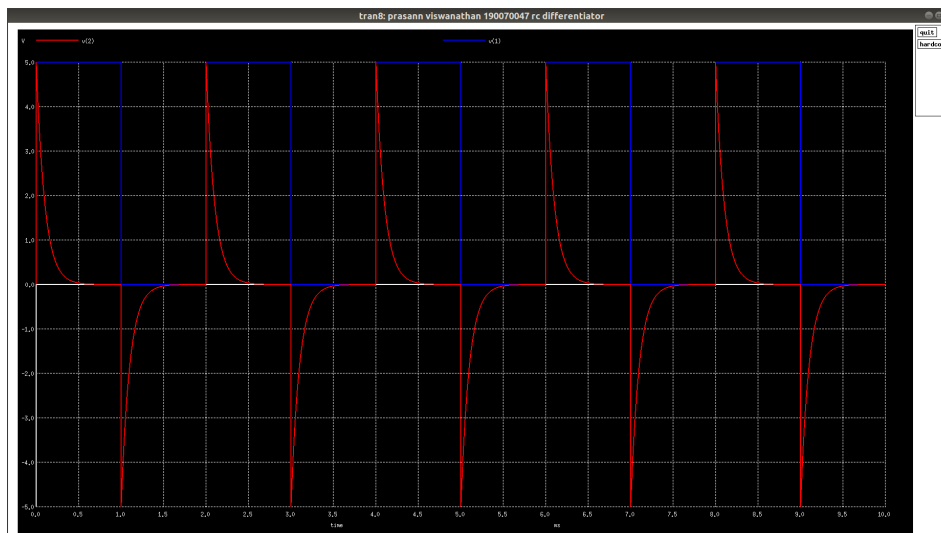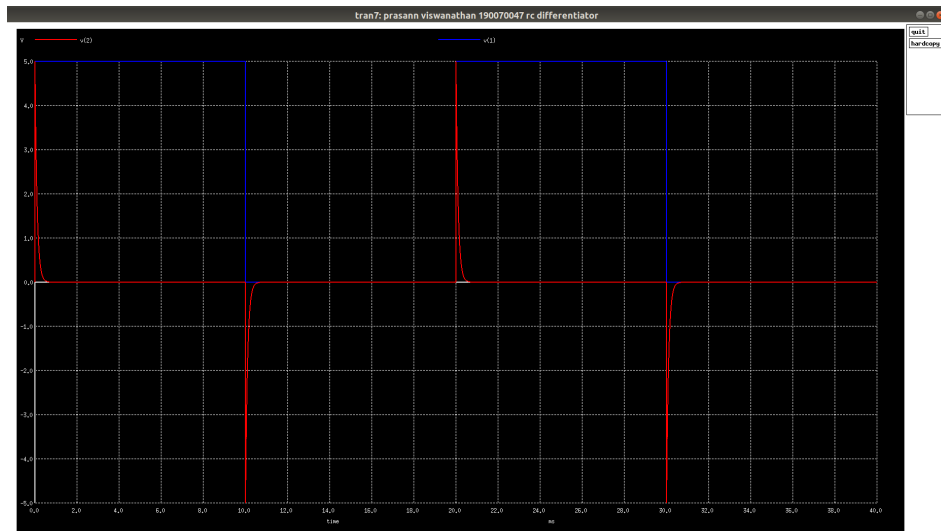

---

### 3. RC Low-pass Filter

a. Circuit Diagram:

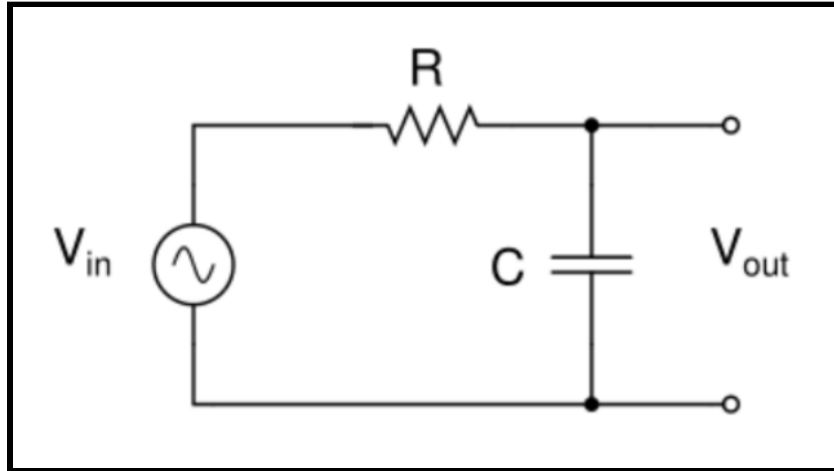

b. ngspice code:


```
Prasann Viswanathan 190070047 RC Low-pass Filter

r1 1 2 10k
c1 2 0 0.1u
v_in 1 0 dc 0 ac 1

*analysis command
.ac dec 10 1 10k
.control
run

*display commands
plot vdb(2)
.endc
.end
```


c. Results:

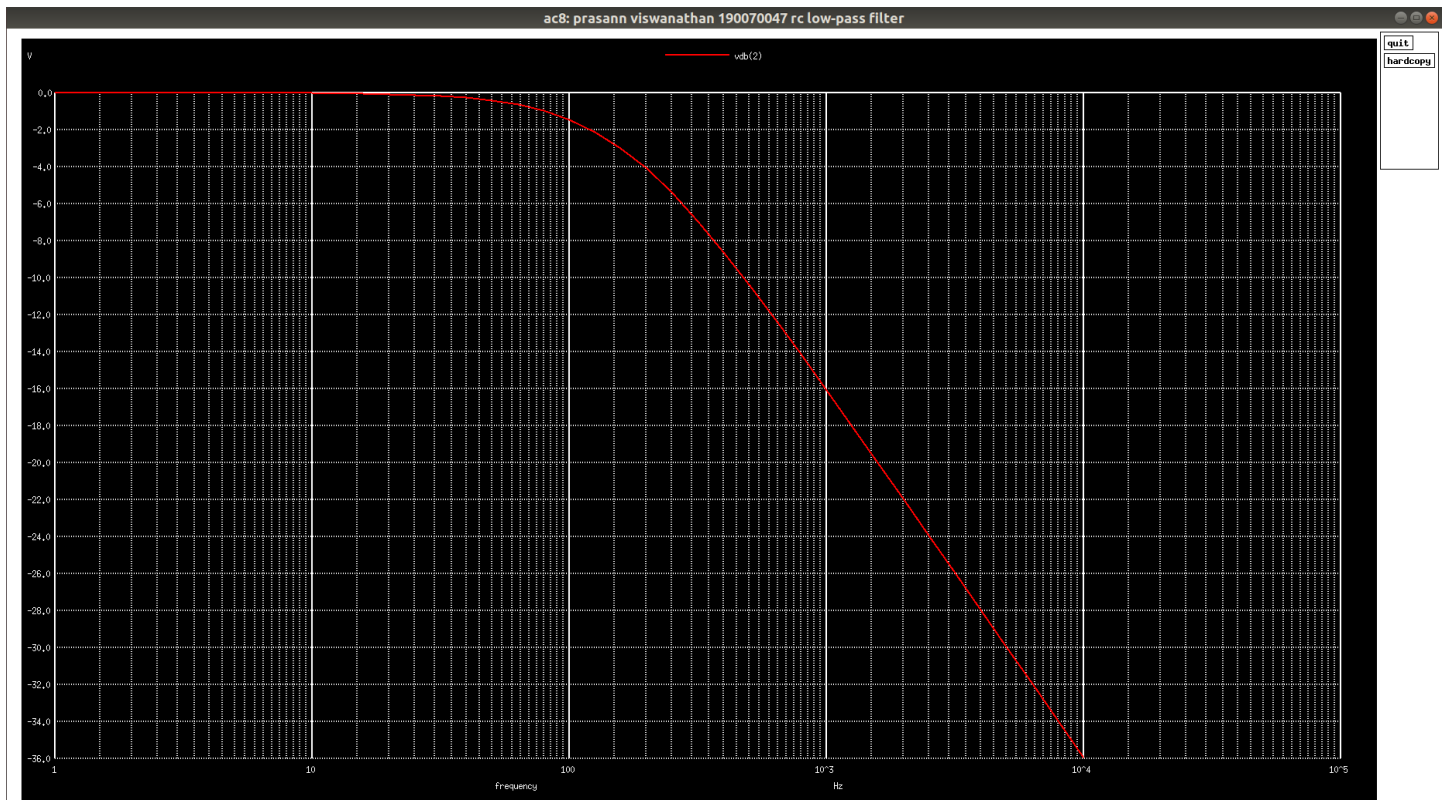

---

## 4. RC High-pass Filter

a. Circuit Diagram:

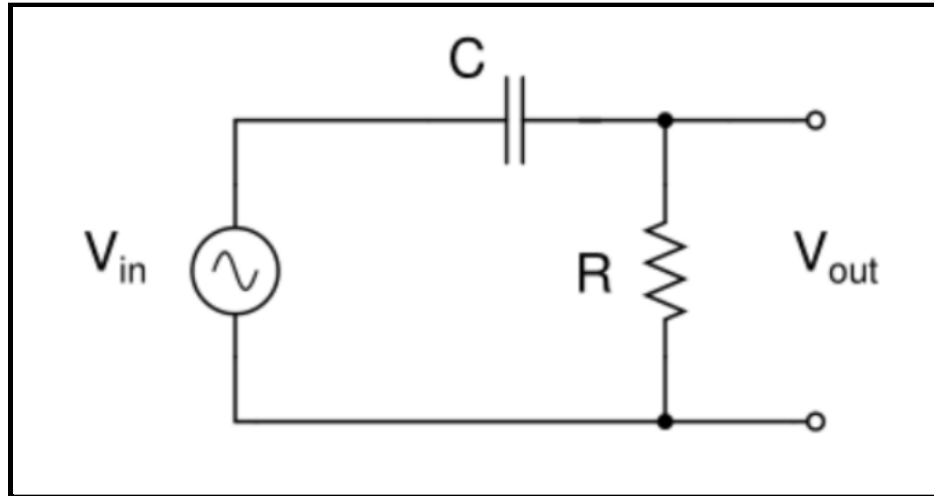

b. ngspice code:


```
Prasann Viswanathan 190070047 RC High-pass Filter
```

```
r1 2 0 10k
c1 1 2 0.1u
v_in 1 0 dc 0 ac 1
```

```
*analysis command
.ac dec 10 1 10k
.control
run
```

```
*display commands
plot vdb(2)
.endc
.end
```


c. Results:

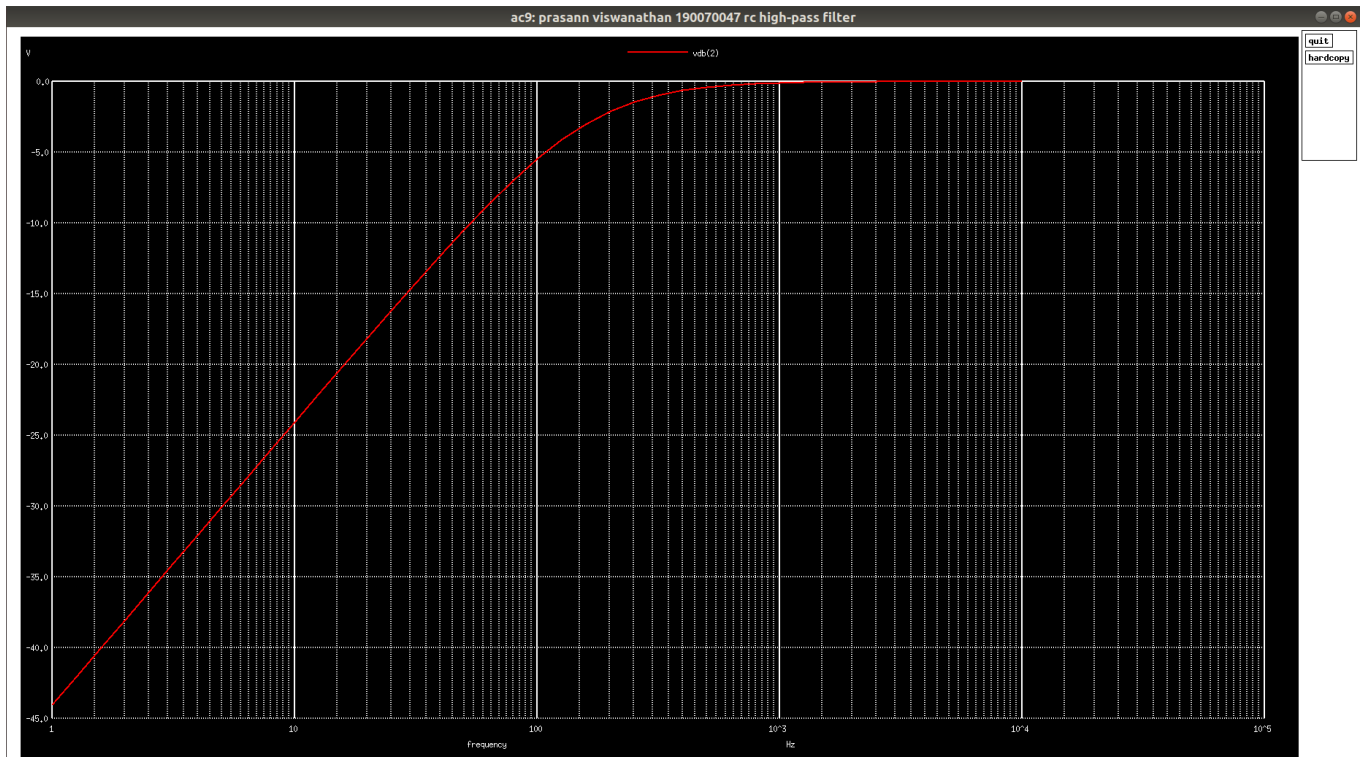



## 5. RC Band-pass Filter

a. Circuit Diagram:

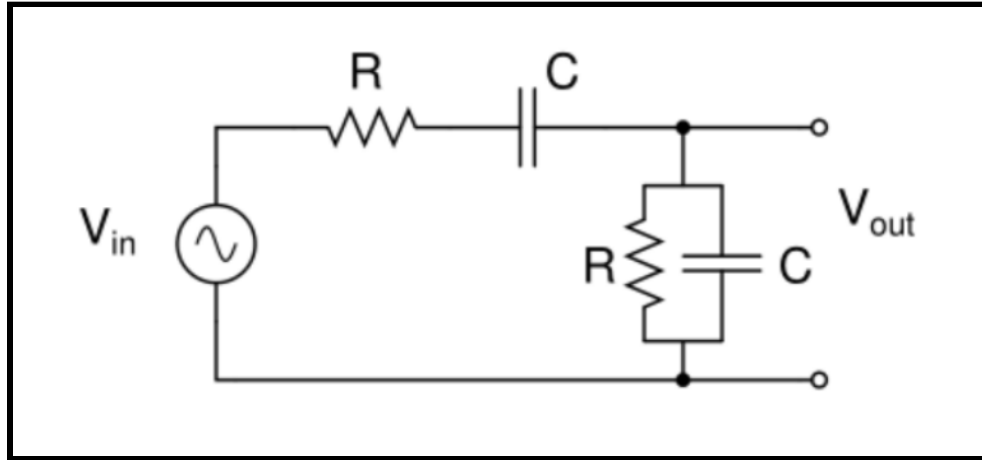

b. ngspice code:


```
Prasann Viswanathan 190070047 RC Bandpass Filter
```

```
r1 1 2 10k
r2 3 0 10k
c1 2 3 0.1u
c2 3 0 0.1u
v_in 1 0 dc 0 ac 1

*analysis command
.ac dec 10 1 10k
.meas ac var max vdb(3)
.control
run

*display commands
plot vdb(3)
.endc
.end
```

c. Results:

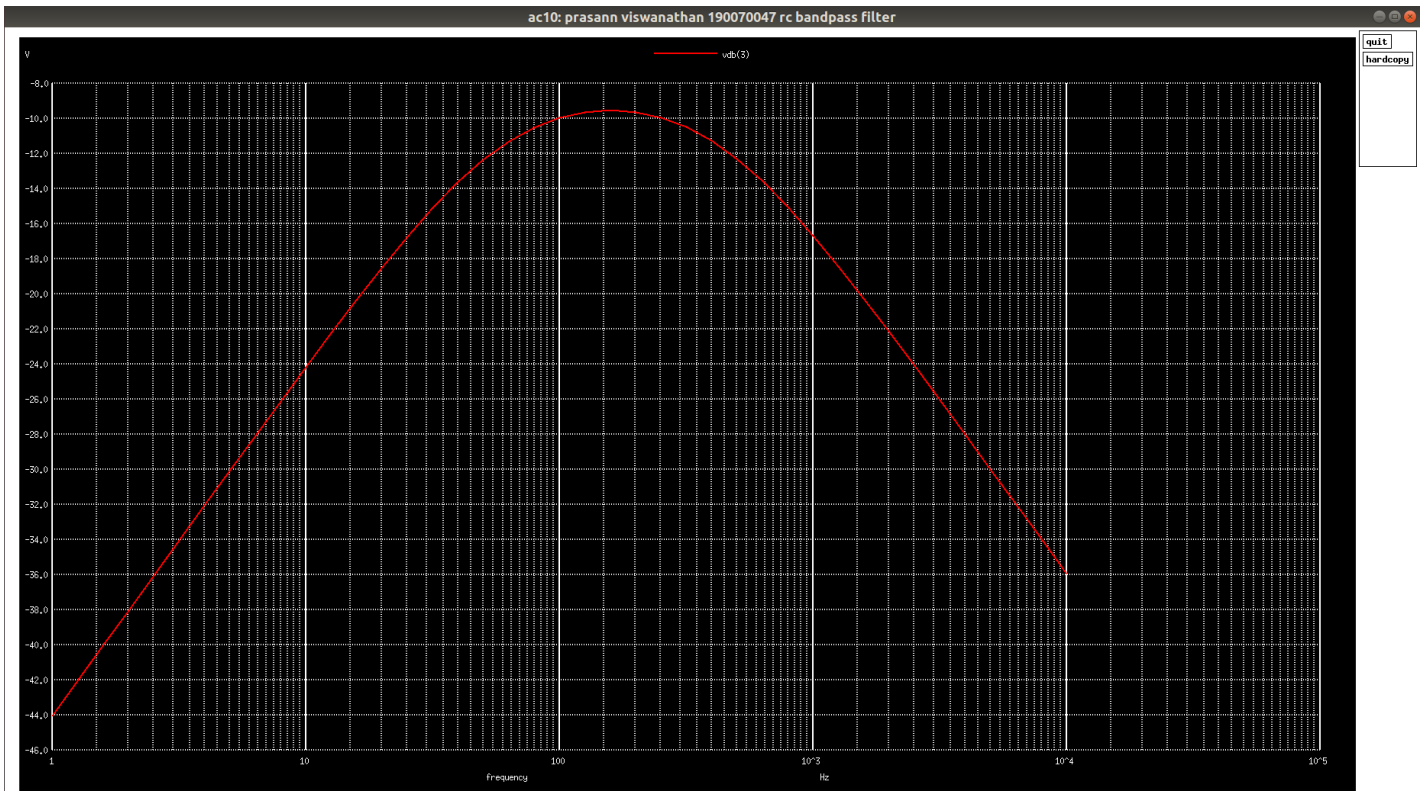

d. Theoretical result:

$$\frac{V_o}{V_{in}} = \frac{R}{1 + sRC} \cdot \frac{1}{\frac{R}{1 + sRC} + \frac{1}{sC} + R} = \frac{R s C}{R s C + 1 + sRC + R s C (1 + sRC)} = \frac{sRC}{1 + 3sRC + s^2 R^2 C^2}$$

Putting  $s = j\omega$  and equating denominator to 0 (Real part)

$$\Rightarrow \omega = \frac{1}{RC} \Rightarrow f_0 = \frac{1}{2\pi RC} = 159.15 \text{ Hz}$$

Peak Amplitude  $= 20 \log(1/3) = -9.54 \text{ dB}$


And cutoff frequency  $\Rightarrow \text{Re}(\text{Denom.}) = \text{Im}(\text{Denom.})$

$$\Rightarrow f_L = 48.18 \text{ Hz} \quad f_H = 525.65 \text{ Hz}$$

---

## 6. RLC Band-pass Filter

a. Circuit Diagram:

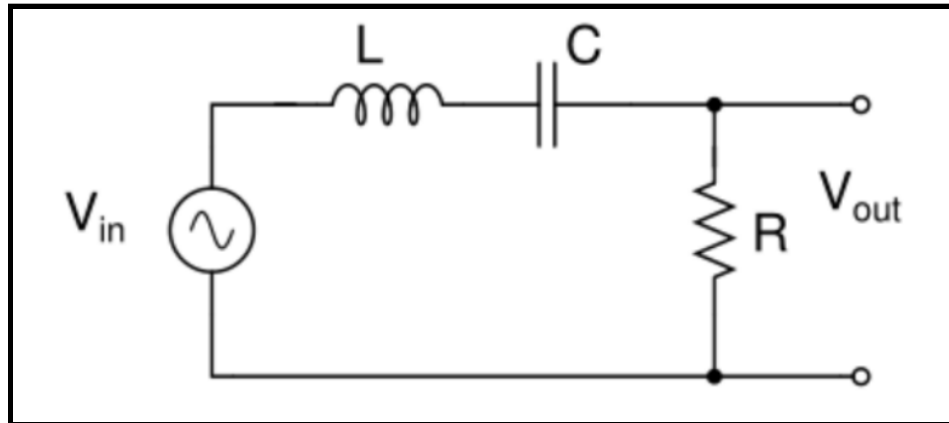

b. ngspice code:


```
Prasann Viswanathan 190070047 RLC Bandpass Filter
```

```
r1 3 0 1k
c1 2 3 0.1u
l1 1 2 10m
v_in 1 0 dc 0 ac 1

*analysis command
.ac dec 10 1 1000k
.meas ac var max vdb(3)
.control
run

*display commands
plot vdb(3)
.endc
.end
```

c. Results:

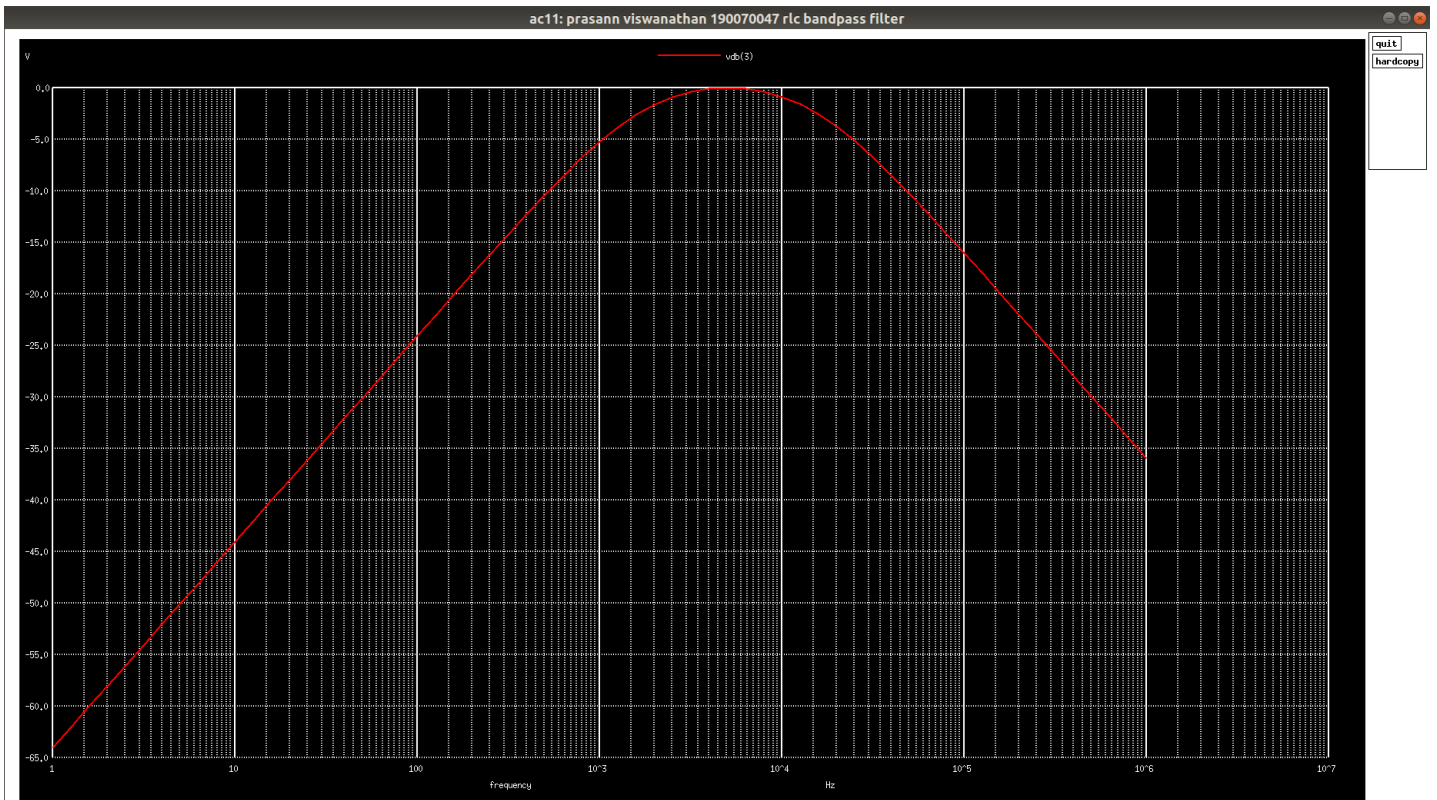

d. Theoretical result:

$$\begin{aligned} \frac{V_o}{V_{in}} &= \frac{R}{R + sL + \frac{1}{sC}} = \frac{sRC}{sRC + s^2LC + 1} \\ &= \frac{j\omega RC}{1 + j\omega RC - \omega^2 LC} \end{aligned}$$

$$\Rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}} = 5032.9 \text{ Hz}$$

Peak amplitude =  $20 \log(1) = 0 \text{ dB}$

And  $f_L = 1457.98 \text{ Hz}$        $f_H = 17373.48 \text{ Hz}$

---

## **Major Learnings from this experiment:**

1. Learnt ngspice syntax
2. Comparing simulations and theoretical results.

## **Challenges Faced:**

1. Had to research .meas command for cutoff frequency values

## **Questions or Clarifications:**

None